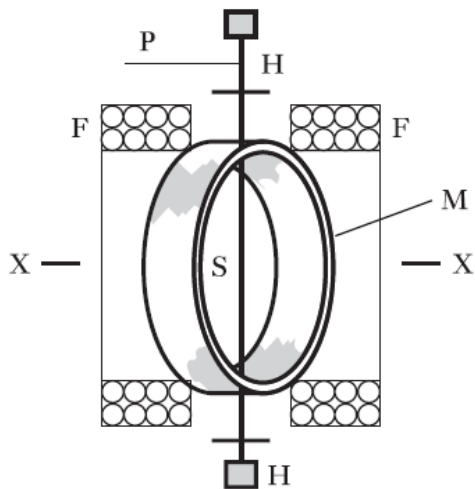




# AC AND NULL METHOD ANALOG MEASURING INSTRUMENTS

# Electrodynamic (Dynamometer) Instrument

- Action of this type of instrument depends upon electromagnetic force exerted between fixed and moving coils carrying current







Deflecting force on each side of M

$\propto$  (current in M)

$\times$  (density of magnetic field due to current in F)

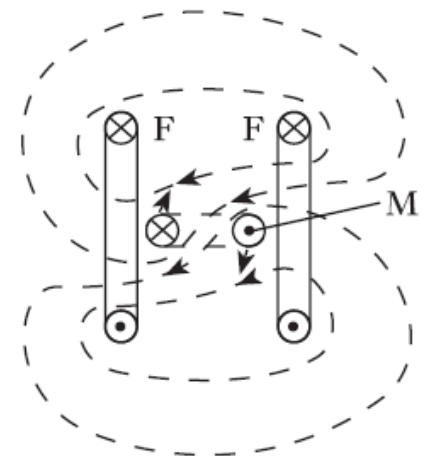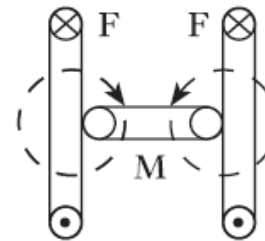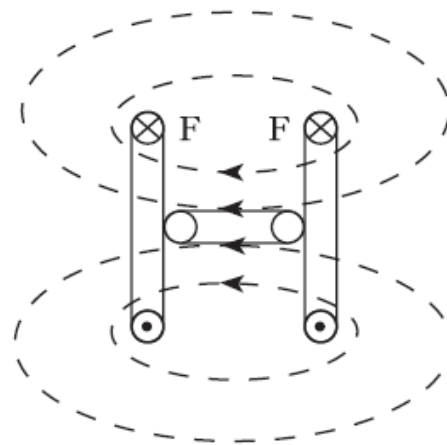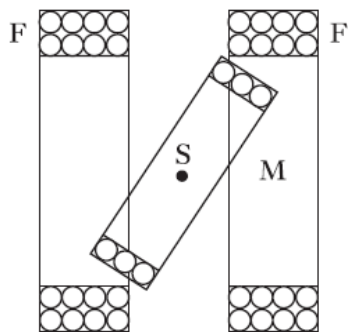$\propto$  current in M  $\times$  current in F



# Electrodynamic (Dynamometer) Wattmeter


- Owing to the higher cost and low sensitivity of dynamometer ammeters and voltmeters, they are rarely used commercially
- However, *electrodynamic or dynamometer wattmeters* are important and commonly employed for measuring power in a.c. circuits
  - ▣ Fixed coils *F* are connected in series with the load, moving coil *M* is connected in series with non-reactive resistor *R* across the supply

Instantaneous force on each side of *M*

- $\propto$  (instantaneous current through *F*)
- $\times$  (instantaneous current through *M*)
- $\propto$  (instantaneous current through load)
- $\times$  (instantaneous p.d. across load)
- $\propto$  instantaneous power taken by load




Average deflecting force on *M*

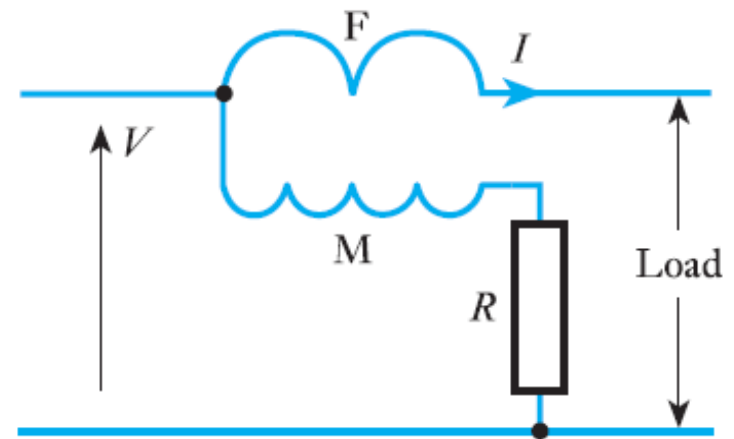- $\propto$  average value of the power over a complete number of cycles


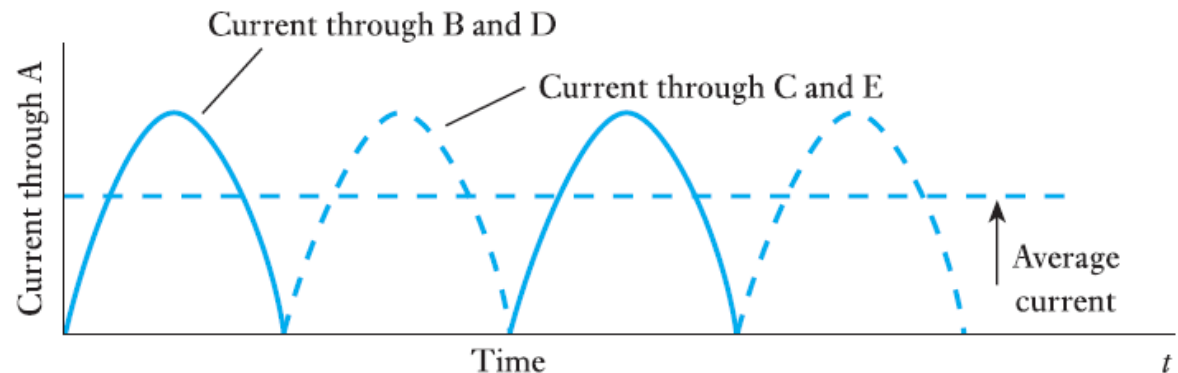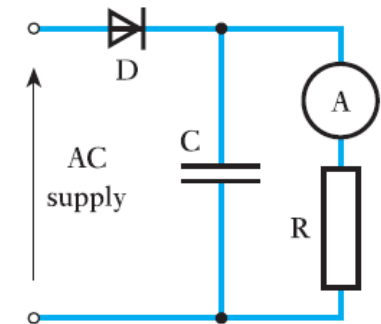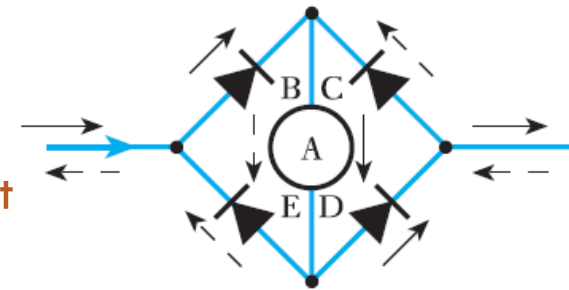
# Rectifier AC Ammeters and Voltmeters

- Rectifier is used to convert AC current into unidirectional current
  - ▣ Mean value is measured using MC type instrument
- Main advantage: far more sensitive than other types of AC voltmeter and can be incorporated in universal instruments (e.g., Avometer)
  - ▣ Enabling MC instrument to be used in combination with bridge rectifier and suitable resistors to measure various ranges of alternating current and voltage




# Oscilloscope

- Oscilloscope is the most important measuring device with graphical display
  - ▣ One of the most powerful diagnostic tools
  - ▣ Commonly used to measure exact wave shape of electrical signal, including the amplitude and frequency
  - ▣ Can also measure quantities such as pulse width, period and rise time, and can compare two signals and measure their relative timing
- Old technology relied on cathode-ray tube (CRT) display
  - ▣ Cathode Ray Oscilloscope (CRO)
- Modern technology uses LCD or LED screens

# Cathode-Ray Tube



- Cathode-ray tube was an important component of both cathode-ray oscilloscope (CRO) and old TVs
  - ▣ CRO now known as analog oscilloscopes to distinguish them from the now almost universally used digital oscilloscope

<b>C</b>	Indirectly heated cathode
<b>G</b>	Control grid with negative bias
<b>A1/A2</b>	Anode discs
<b>F</b>	Focusing electrode
<b>X</b>	Horizontal deflection plates
<b>Y</b>	Vertical deflection plates
<b>S</b>	Fluorescent screen
<b>B</b>	Glass bulb evacuated

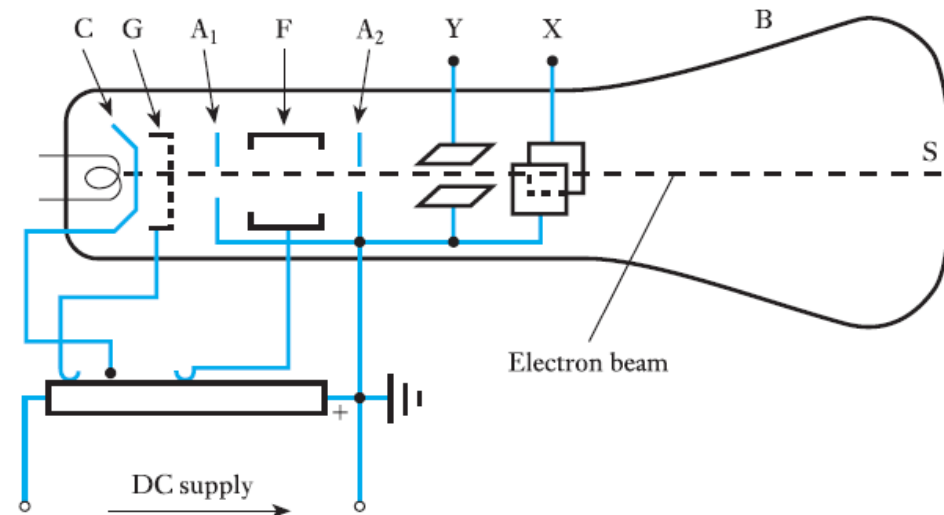

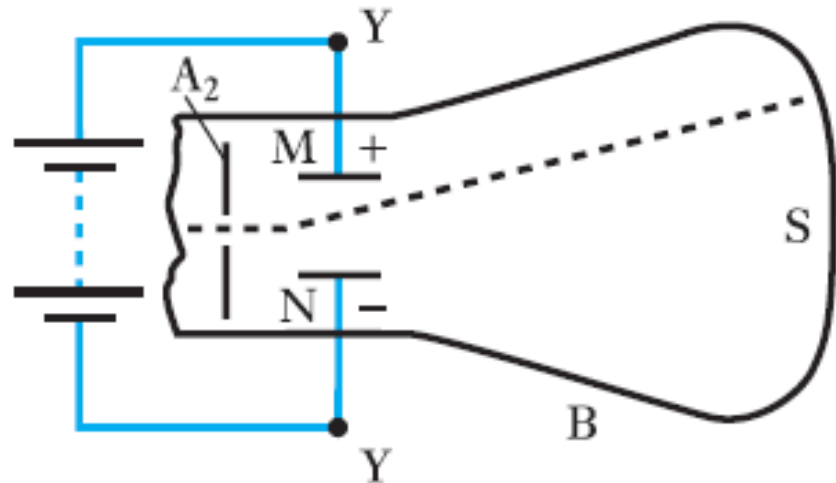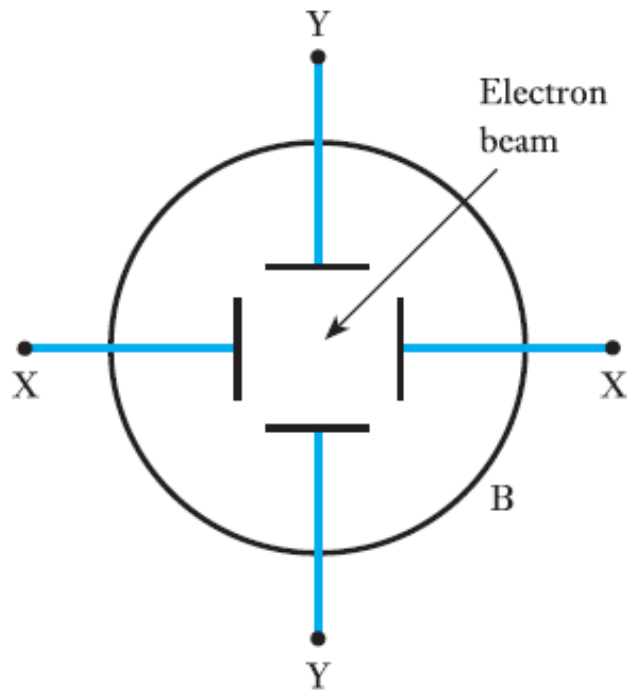
# Cathode-Ray Tube

- **Electron lens:** combination of A1, A2 and F
- **Electron gun:** system of electrodes producing the electron beam
- **Electrostatic deflection systems of cathode-ray tube:** plates X and Y


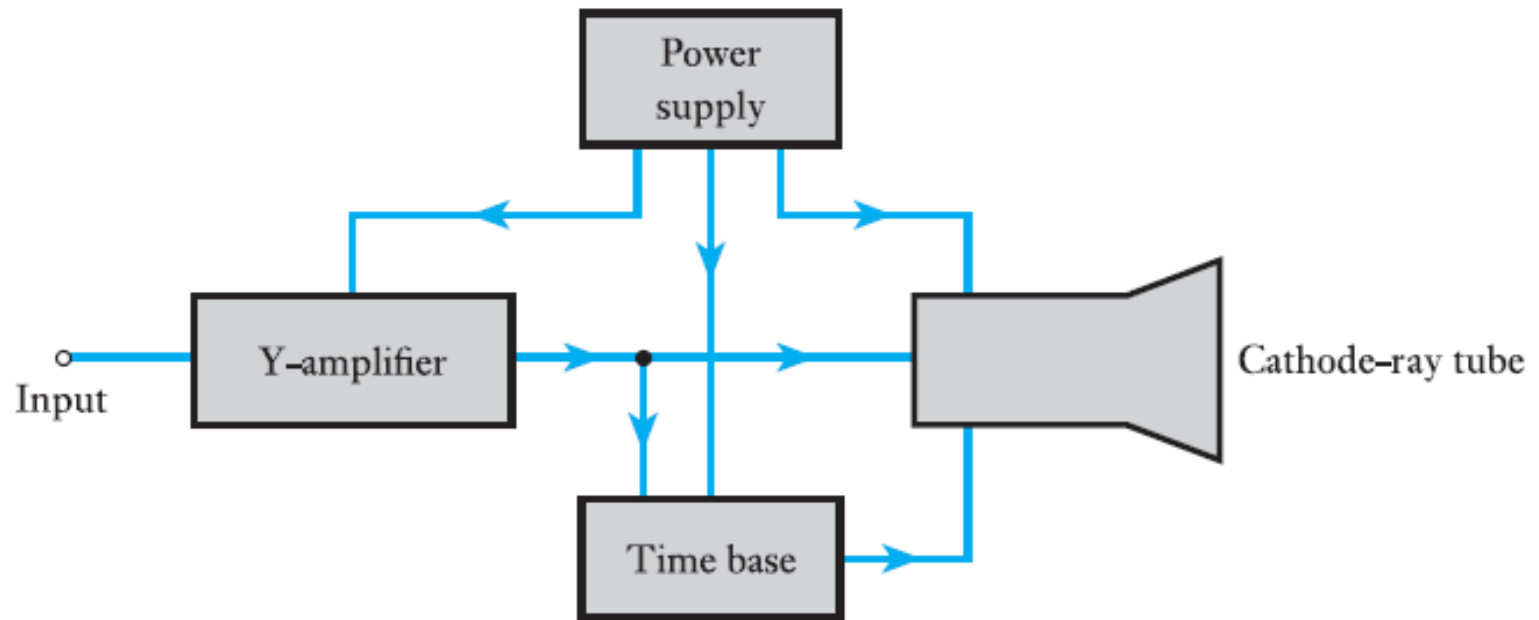
# Cathode-Ray Oscilloscope (CRO)


- Input signal is amplified by Y-amplifier and causes beam to be driven up and down screen of CRT in Y direction
- Time base moves beam across the screen of the tube, in X-direction







# Cathode-Ray Oscilloscope (CRO)

## □ Detailed diagram

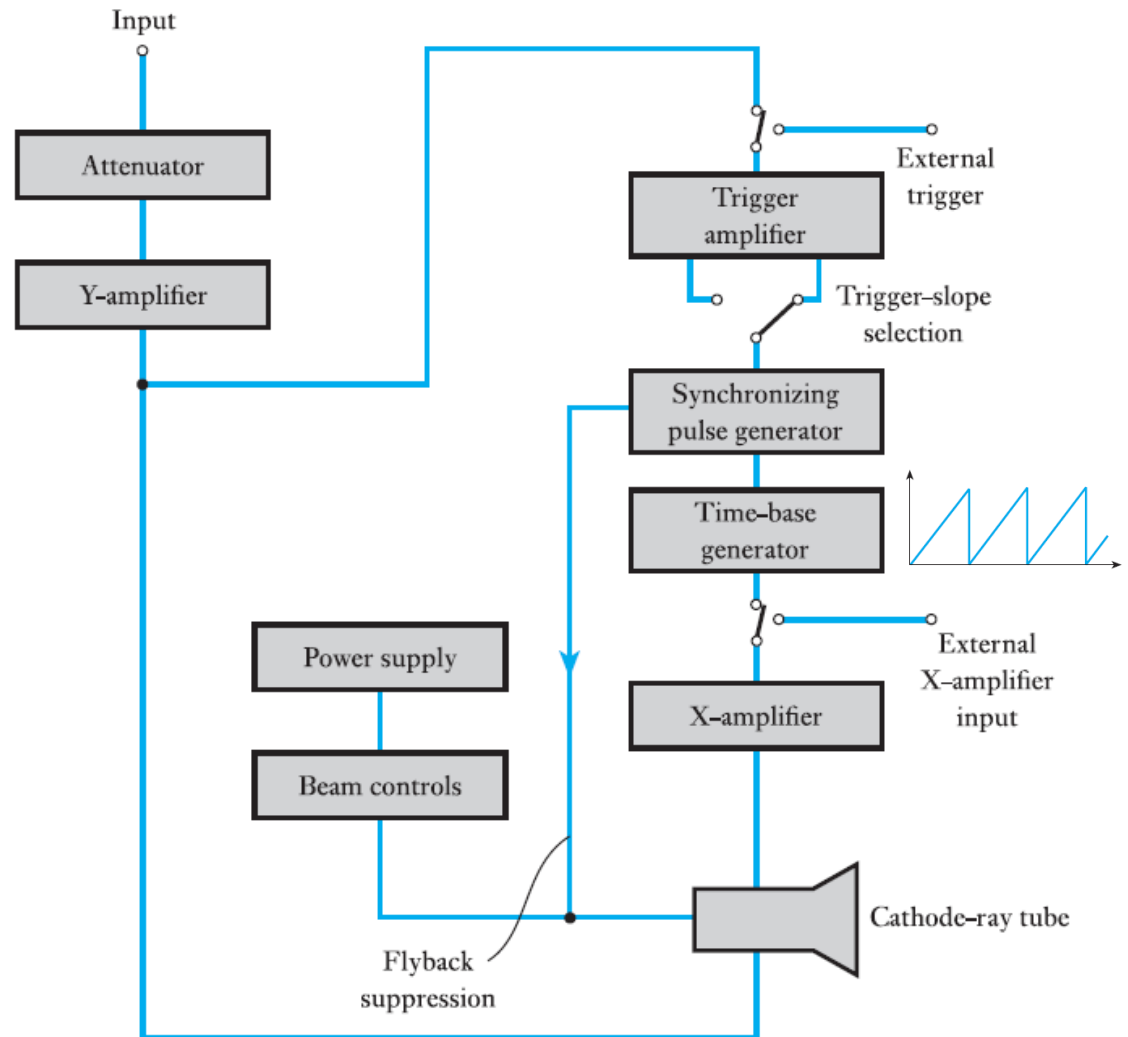

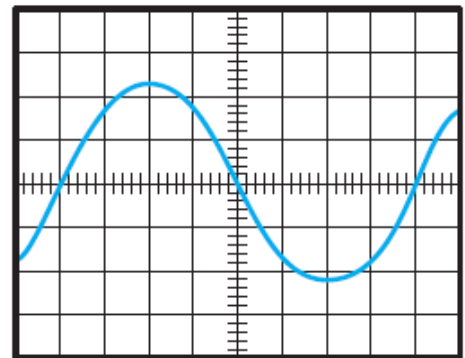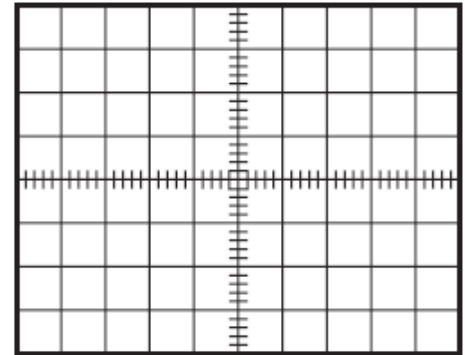
# Waveform Measurement with CRO

- To aid observation of display on CRO, set of squares is marked on the transparent screen cover termed **graticule**
  - ▣ Graticules are marked out with a 1 cm grid and are generally 10 cm across by 8 cm high
  - ▣ To avoid parallax error, always observe trace directly through graticule and not from the side
- Ex: Let vertical control be set to 2 V/cm and time-base control to 500  $\mu\text{s}/\text{cm}$ :
  - ▣ Peak-to-peak height of display is 4.8 cm, hence the peak-to-peak voltage is  $4.8 \times 2 = 9.6 \text{ V}$
  - ▣ length of one cycle of display is 8.0 cm, hence the period of the waveform is  $8 \times 500 \times 10^{-6} = 4 \text{ ms}$  and frequency of signal is 250 Hz



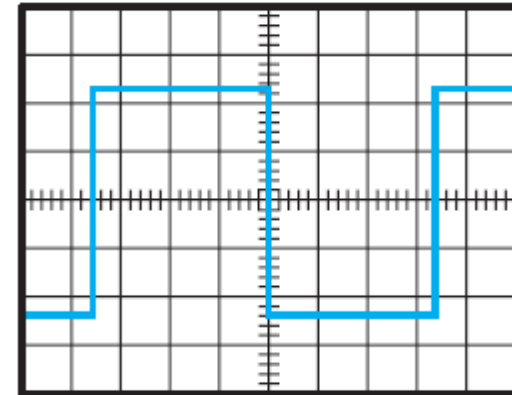
# Examples

The trace displayed by a CRO is as shown in Fig. 45.20(a). The signal amplitude control is set to 0.5 V/cm and the time-base control to 100 s/cm. Determine the peak-to-peak voltage of the signal and its frequency.



(a)

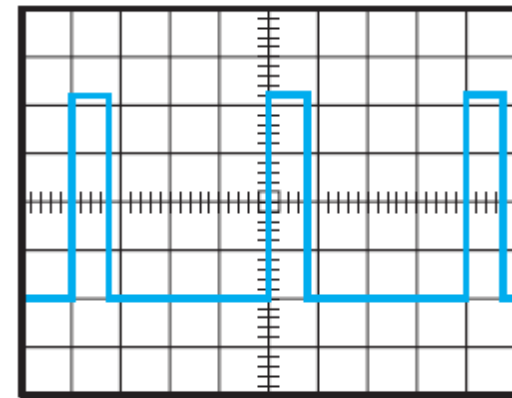An oscilloscope has the display shown in Fig. 45.20(b). The signal amplitude control is set to 0.2 V/cm and the time-base control to 10 s/cm. Determine the mark-to-space ratio of the pulse waveform and the pulse frequency. Also determine the magnitude of the pulse voltage.




(b)

← Space →      ← Mark →

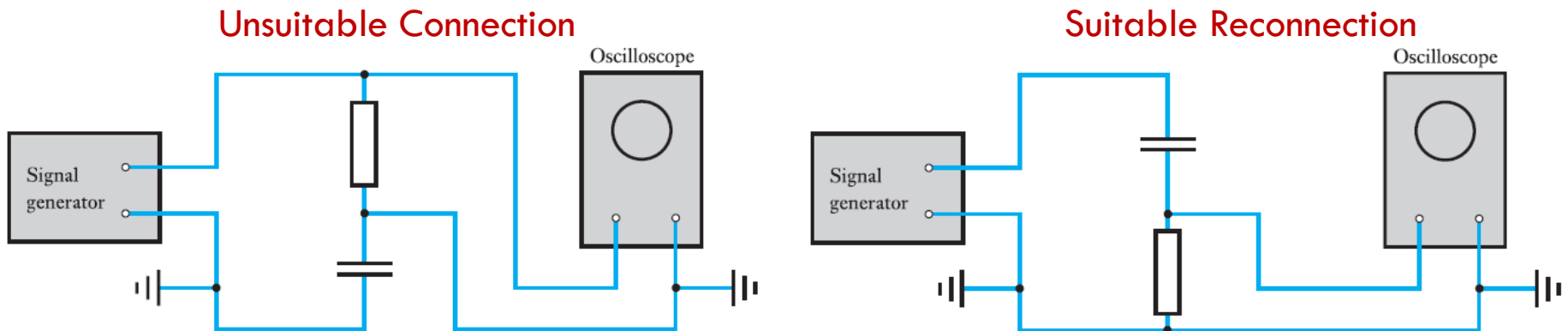
# Oscilloscope Connection

- Most oscilloscopes operate with the body or chassis of the instrument at earth potential
- Also, most oscilloscopes are connected to the signal source by means of a coaxial cable, the outer conductor of which is connected to the body of the oscilloscope and is therefore at earth potential
- It follows that one of the connections from the oscilloscope will connect one terminal of the signal source to earth


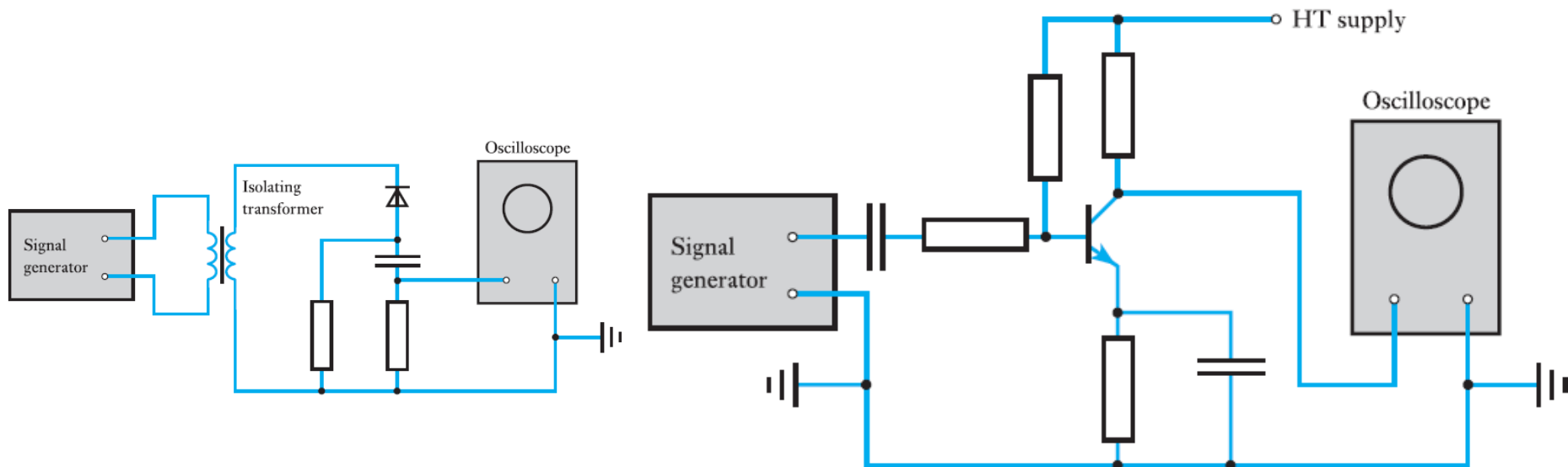
# Oscilloscope Connection Challenges

- ❑ Amplifier transistor circuit shown could not be reconnected in order to observe the voltage across the base-collector junction
- ❑ Method 1: Isolation of the source from earth
- ❑ Method 2: Isolation of the load from the source
- ❑ Method 3: Dual-trace measurements
- ❑ Method 4: Isolation of the oscilloscope from earth



# Null method: Measurement of Resistance by Wheatstone Bridge


- Bridge has two known resistances P and Q, known variable resistance R and the unknown resistance X
- Battery B is connected through switch S1 to C and F
- Galvanometer G, variable protection resistor A and switch S2 are in series across D and E
- With S1 and S2 closed, R is adjusted until there is no deflection on G
  - ▣ Very accurate because no loading effect is involved

$$PI_1 = RI_2$$

$$QI_1 = XI_2$$

$$\frac{Q}{P} = \frac{X}{R}$$

$$X = R \times \frac{Q}{P}$$

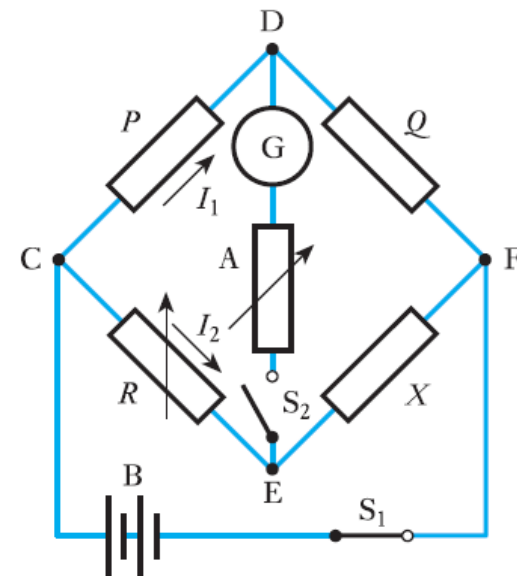


# Null Method: Measurement of Voltage by Potentiometer

- One of the most accurate instruments for measuring voltage
- Slider L position is adjusted until the galvanometer deflection is zero
  - ▣ First time: for  $E_1$  (SC) and find length between M and L ( $l_1$ )
  - ▣ Second time: for  $E_2$  (Unknown) and find length between M and L ( $l_2$ )
- Main advantage: no current flows at balance
  - ▣ Very accurate because no loading effect is involved

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$



$$E_2 = E_1 \times l_2 / l_1$$

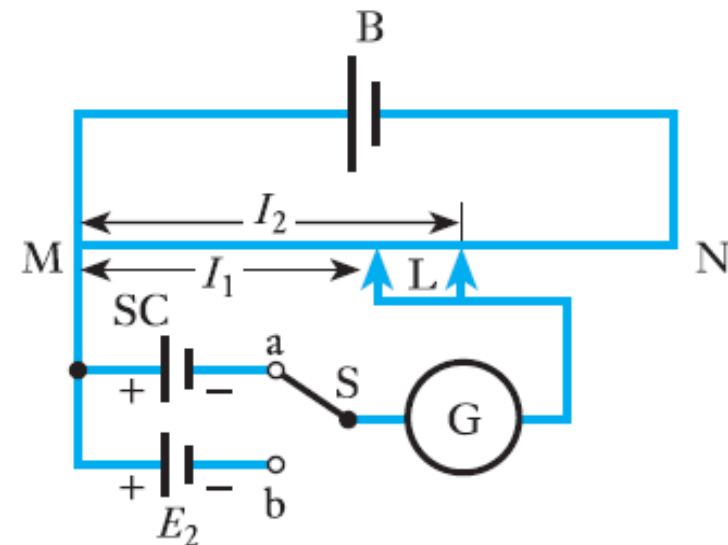

# Suggested Readings and Exercises

- Hughes textbook – Chapter 45.8, 45.9, 45.10, 45.11, 45.12, 45.13 and Chapter 46.7, 46.9, 46.10, 46.11
- Exercise 45 (Hughes)
  - ▣ Problems 6, 8
- Exercise 46 (Hughes)
  - ▣ Problems 11, 15, 16, 17, 18, 23