

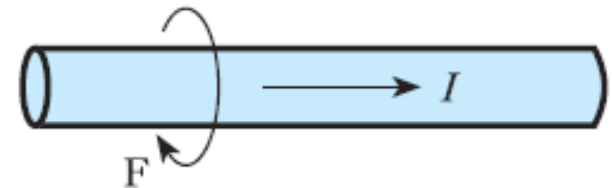
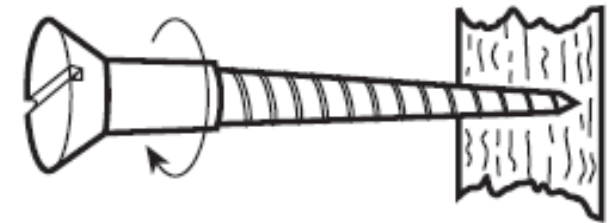
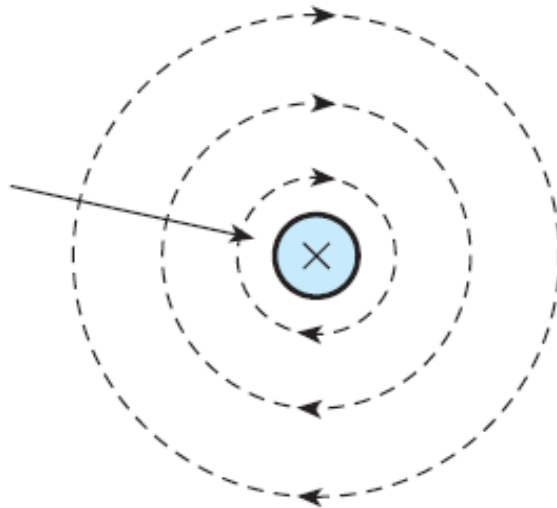


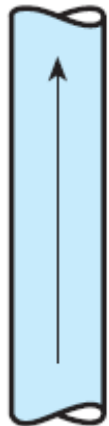

DC ANALOG MEASURING INSTRUMENTS


Basics: Magnetic Field Due to Electric Current

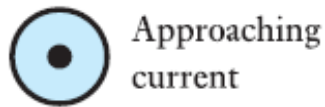- When conductor carries electric current, magnetic field is produced around that conductor
 - ▣ **Right-Hand Screw rule**



Basics: Force on Current-Carrying Conductor

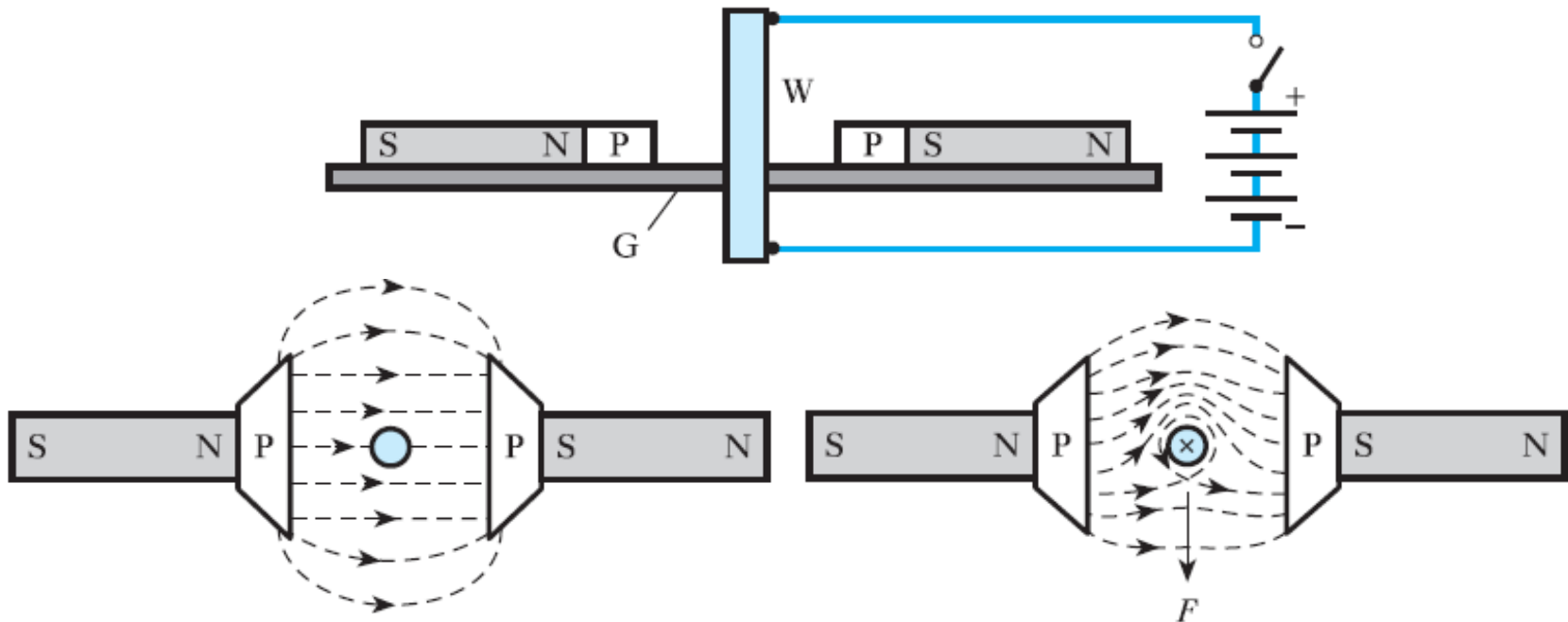- When a current-carrying conductor is placed in a magnetic field, the field from the current distorts the original field
 - ▣ Distorted flux acts like stretched elastic cords: lines of flux try to return to the shortest straight line paths thereby exerting force F urging the conductor out of the way



Basics: Force Determination


- Assume conductor carrying current at **right angle** to magnetic field
- Direction: Left-Hand Rule
- Magnitude: F [newtons] \propto flux density $\times l$ [metres] $\times I$ [amperes]

$$F = BIl$$

B : magnetic flux density in Tesla (T)

l : Length of conductor (m)

I : Current (A)

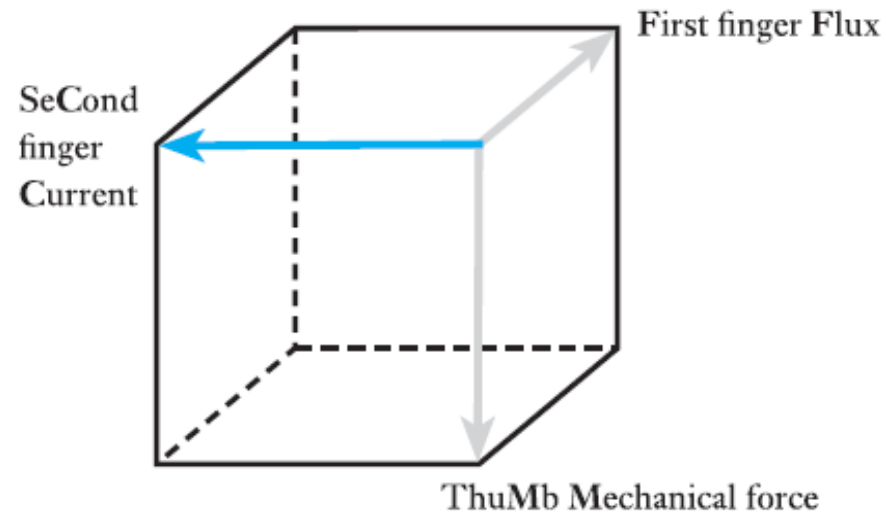




A conductor carries a current of 800 A at right angles to a magnetic field having a density of 0.5 T. Calculate the force on the conductor in newtons per metre length.

Analog Measurement Instruments

- Indicating analogue instruments possess three essential features:
 1. A **deflecting** device whereby a mechanical force is produced by the electric current, voltage or power.
 2. A **controlling** device whereby the value of the deflection is dependent upon the magnitude of the quantity being measured.
 3. A **damping** device to prevent oscillation of the moving system and enable the latter to reach its final position quickly.

Moving-Coil (MC) Instrument

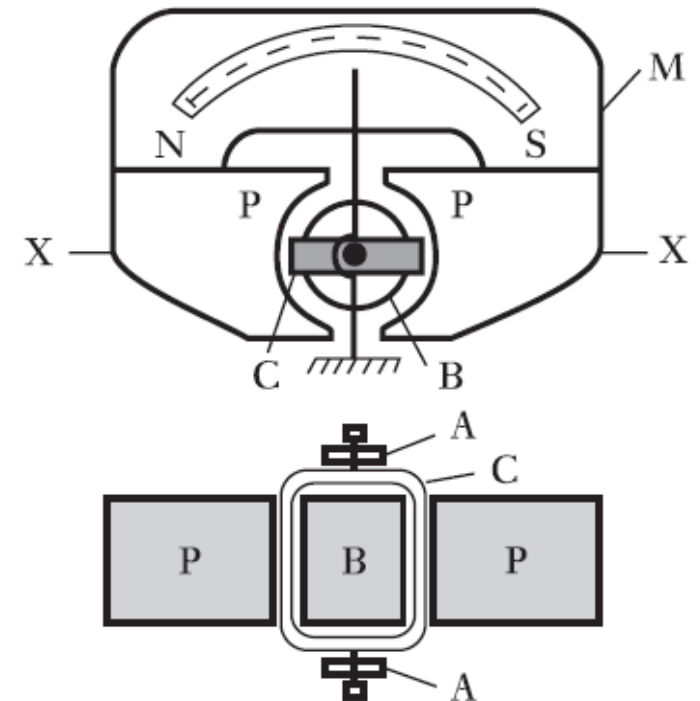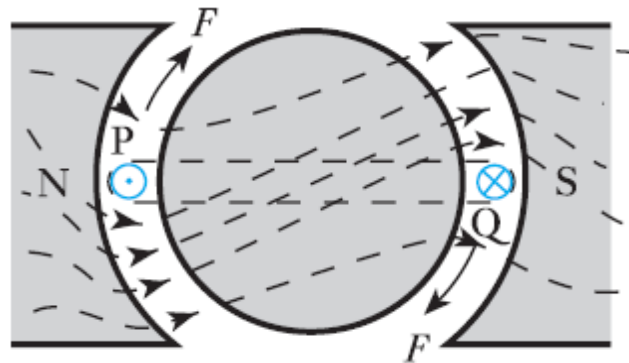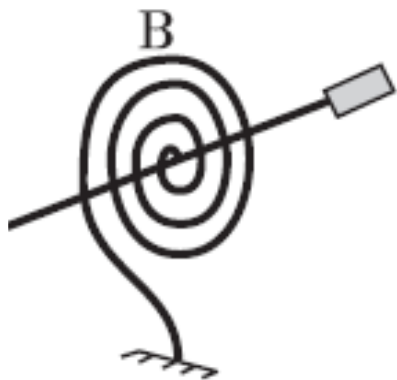- MC Instrument is an analog electromechanical transducer that produces a rotary deflection of some type of pointer in response to electric current flowing through its coil
 - ▣ Instrument for detecting and measuring electric current (Ammeter)
 - ▣ Deflecting: electromechanical force
 - ▣ Controlling: spiral spring
 - ▣ Damping: eddy current



Moving-Coil Instrument Analysis

- Deflecting Force: $F = B I$
- For N turns and coil width w (where coil area $A = l w$), resultant deflecting torque $= N F w$, such that:

$$T_{EM} = N B I A$$



- Spring torque is given as:

$$T_{SP} = k \theta$$

- ▣ $k =$ spring constant

- At equilibrium, torques balance: $T_{EM} = T_{SP}$

$$\theta = (N B A / k) I$$

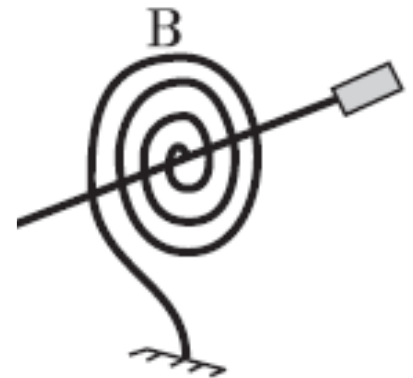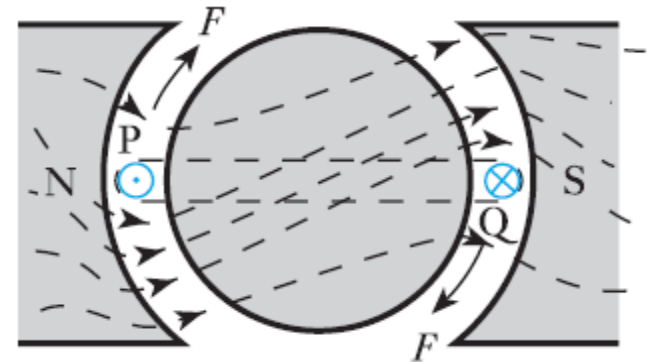




Example

A moving coil has following parameters: Area $A = 2 \text{ cm}^2$, $B = 0.2 \text{ Tesla}$, coil resistance $= 50 \Omega$, current $I = 1 \text{ mA}$. Calculate:

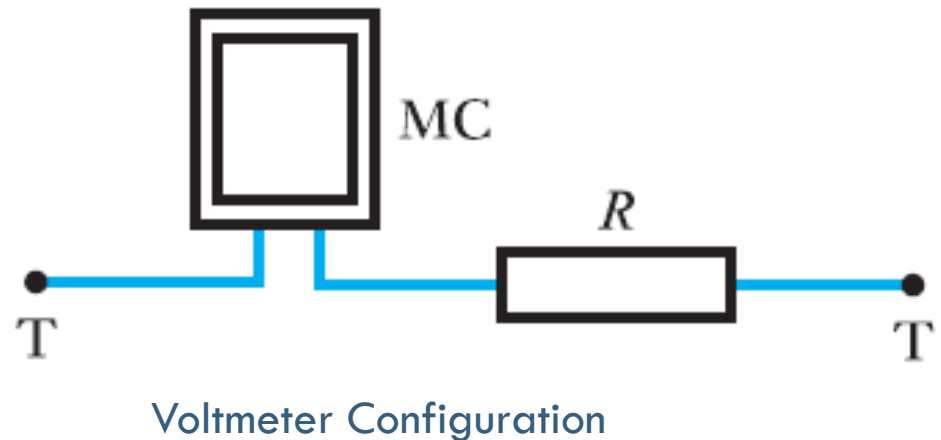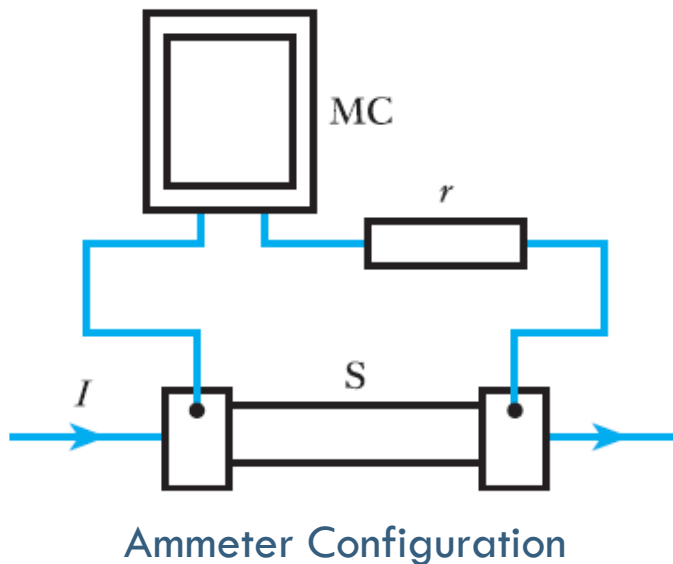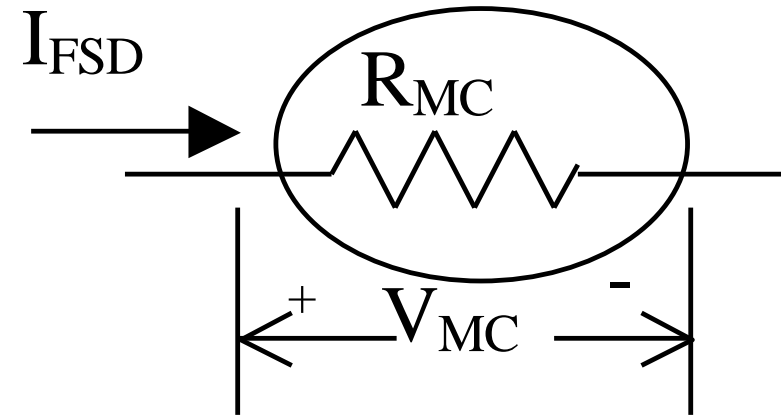
- a. Power dissipated by coil
- b. The electromagnetic torque established.
- c. Assume the electromagnetic torque is compensated by a spring torque and the spring constant $k = 3.6 \times 10^{-8} \text{ N.m/degrees}$. Find the angle of deflection of the coil at equilibrium

MC in Analog Electrical Measuring Instruments

- MC model:
 - Coil resistance
 - Current for full-scale deflection (FSD)
 - Voltage (derived from the above two)



Basic DC Ammeter

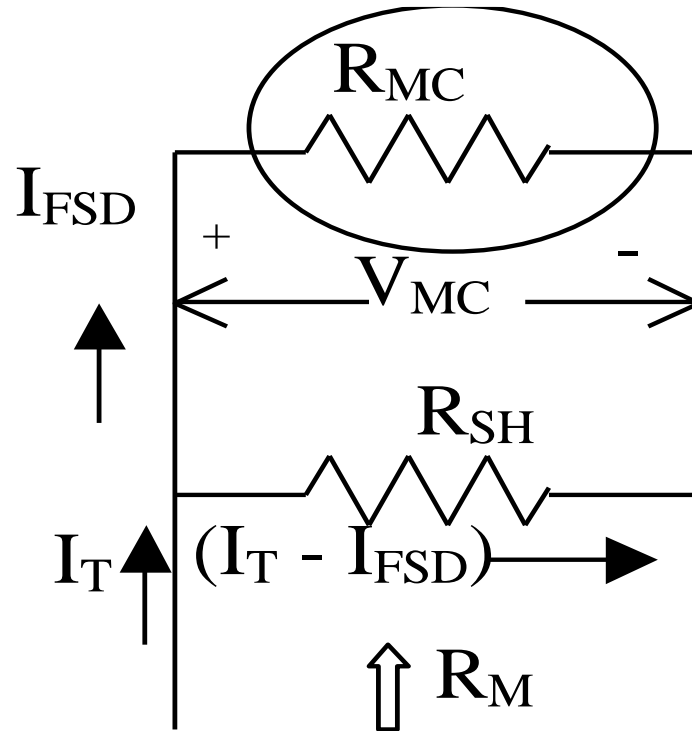


$$V_{MC} = I_{FSD} R_{MC} = (I_T - I_{FSD}) R_{SH}$$


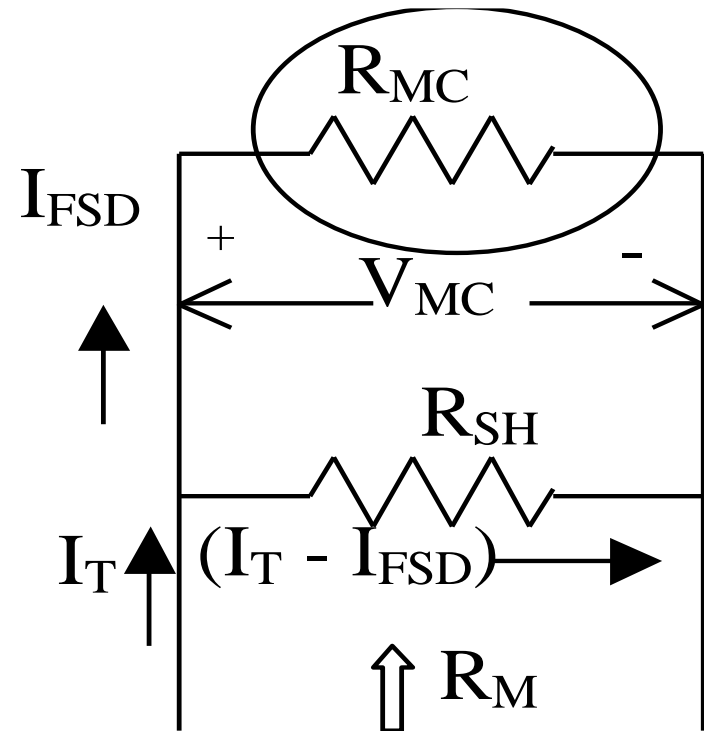
Example

Calculate the multiplying power of a shunt of $200\ \Omega$ resistance used with a galvanometer of $1000\ \Omega$ resistance as shown.


Also, determine the value of shunt resistance to give a multiplying factor of 50.



Multi-Range Ammeter

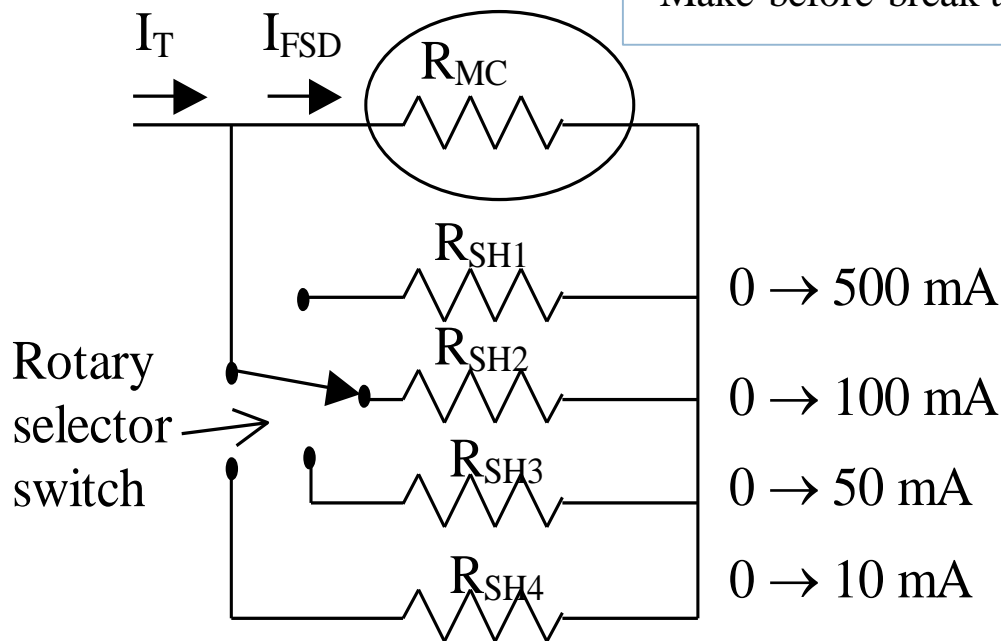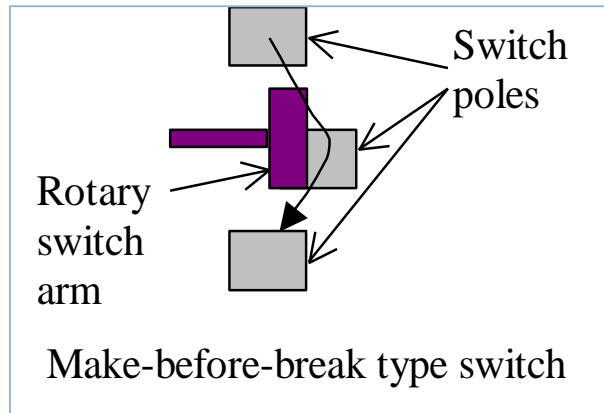

Multi-range ammeter circuit

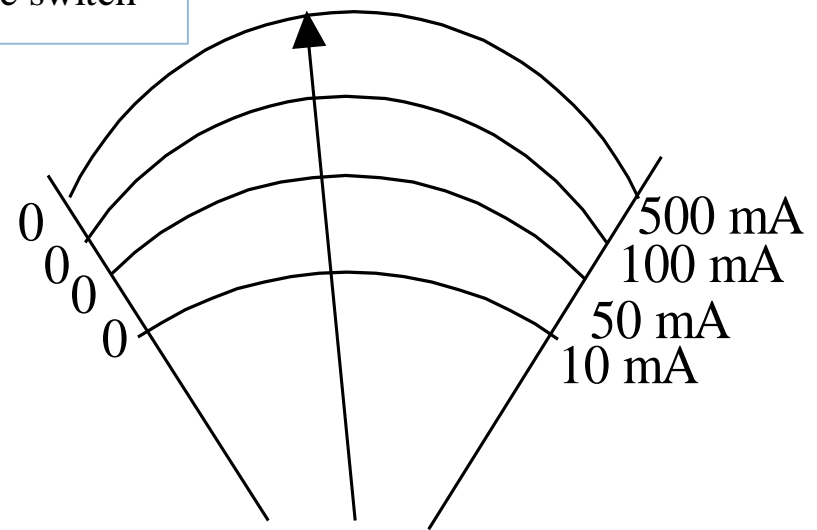


Multi-range ammeter scale

Basic DC Voltmeter

$$V_M = I_{FSD} (R_S + R_{MC})$$


$$R_M = R_S + R_{MC}$$

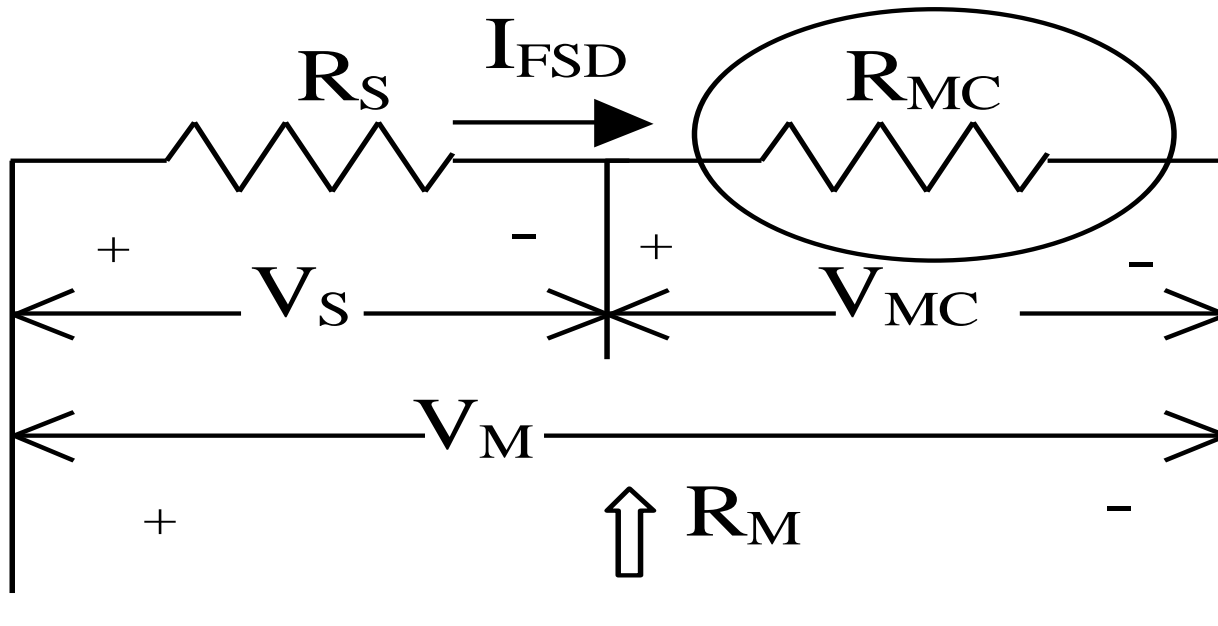Usually $R_S \gg R_{MC}$ \rightarrow $V_M \cong I_{FSD} R_S$






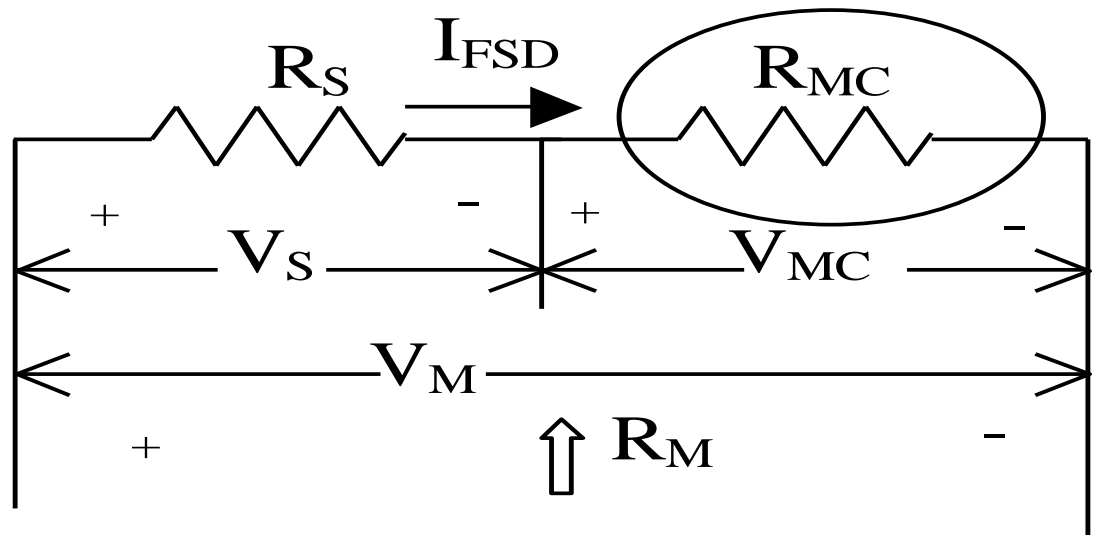Example


- A moving coil instrument gives full-scale deflection of 10 mA when the potential difference across its terminals is 100 mV. Calculate the resistance for full scale reading of 1000 V.




Multi-Range Voltmeter

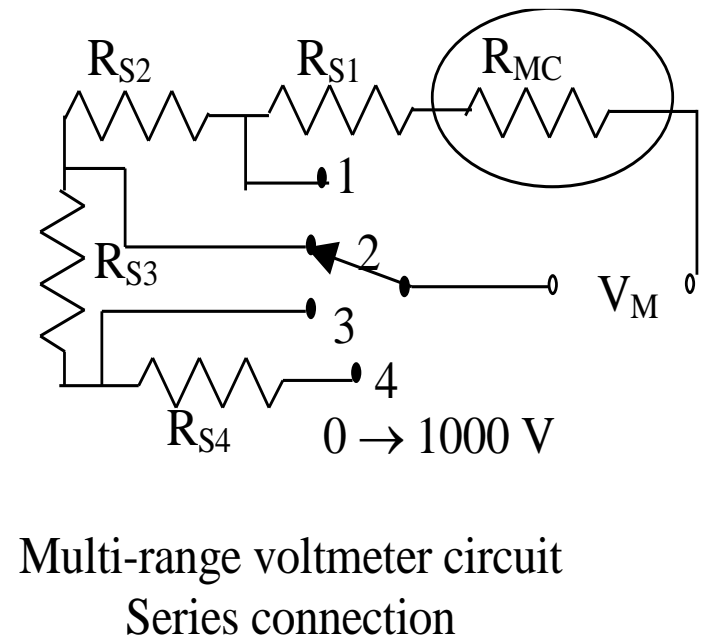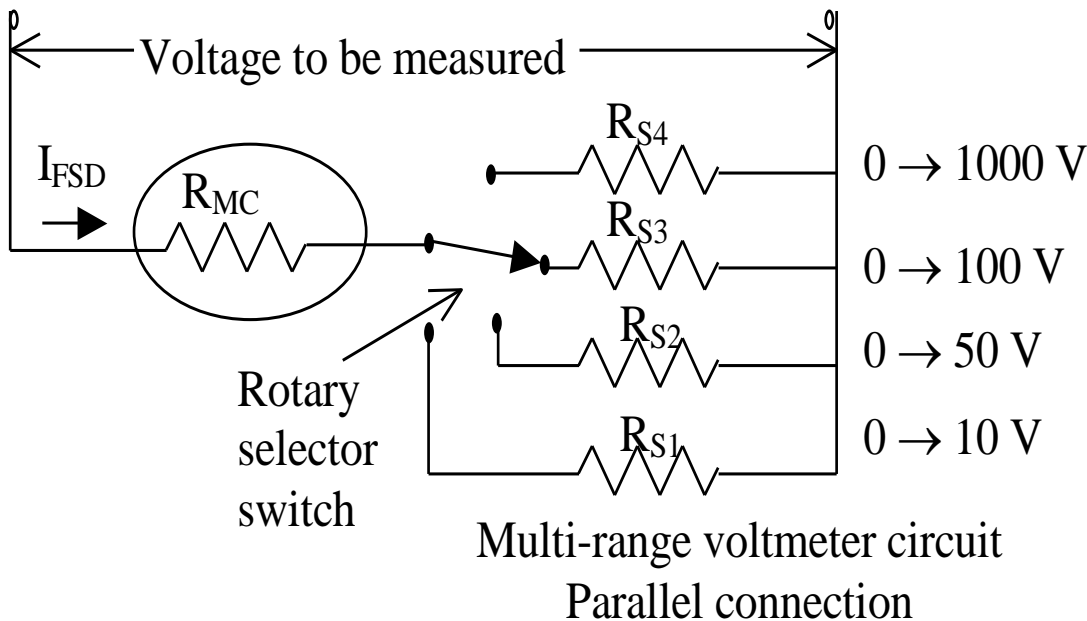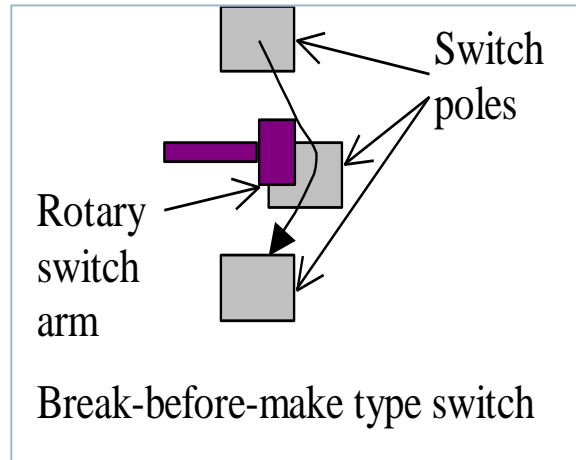

Analog Ohmmeter

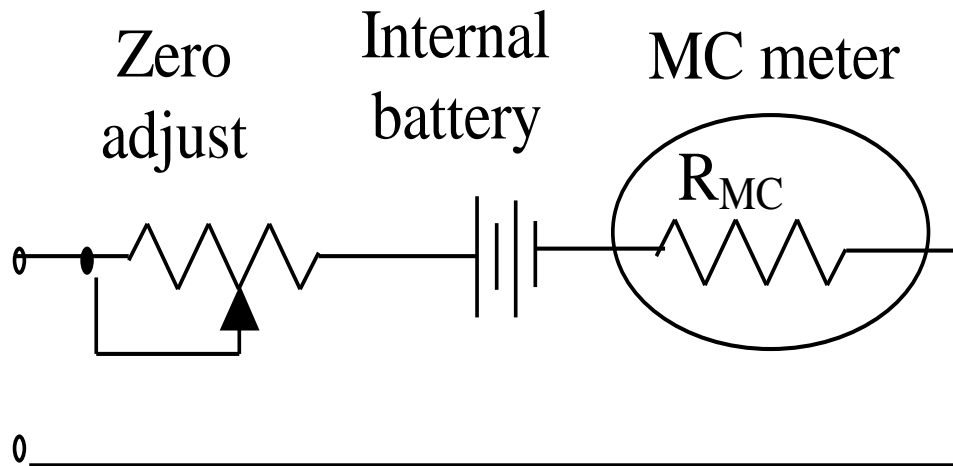


Basic series ohmmeter circuit

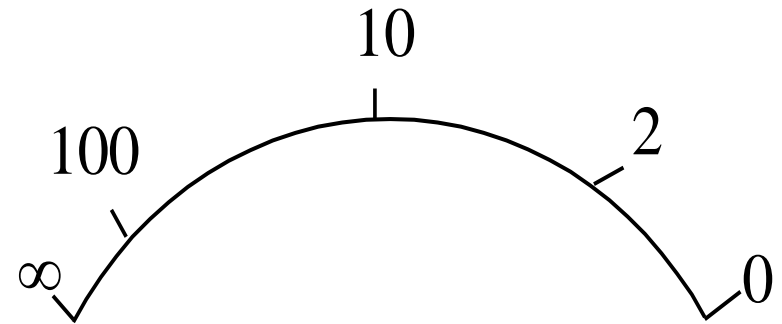


Series ohmmeter scale

Instrument Loading

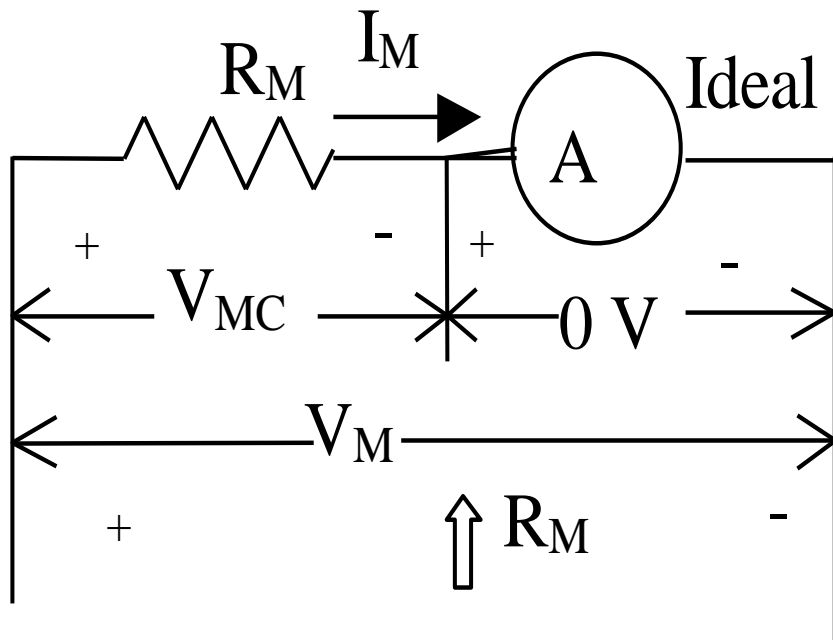


Practical ammeter

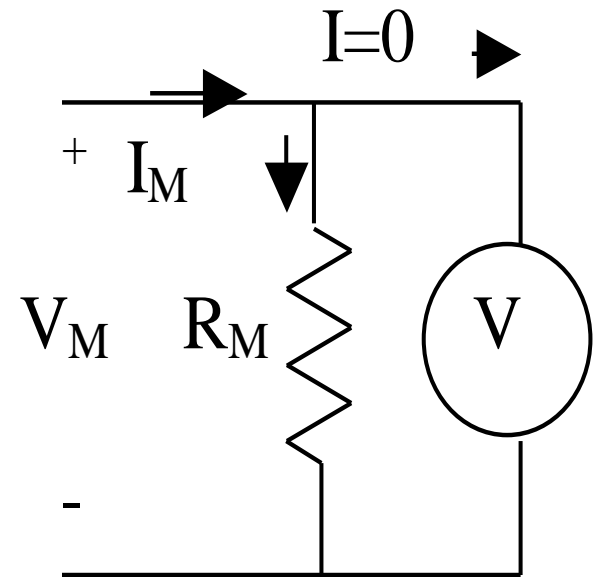

Practical voltmeter

Loading Errors in Ammeters

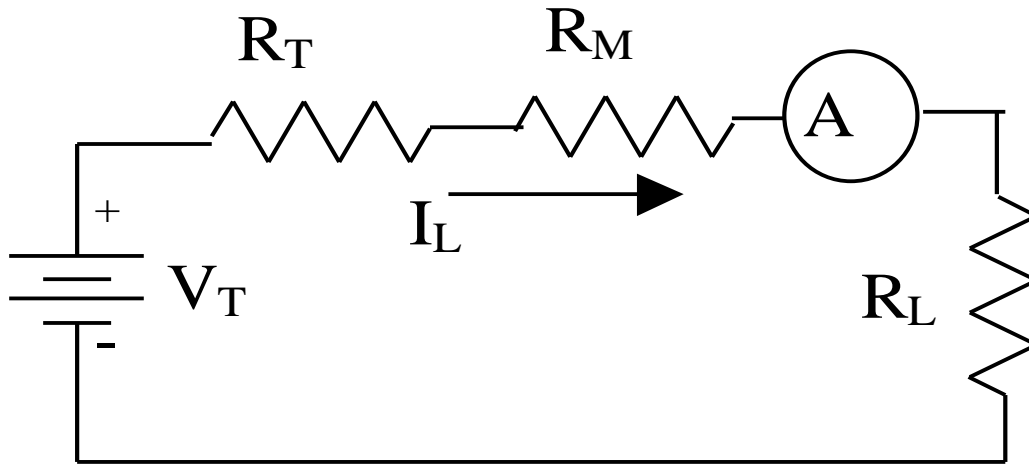


$$I_L = \frac{V_T}{R_T + R_L + R_M}$$

$$I_{LT} = \frac{V_T}{R_T + R_L}$$

$$\% \text{ loading error} = \frac{\text{measured} - \text{true}}{\text{true}} \times 100$$

$$\% \text{ loading error for ammeter} = \frac{\frac{V_T}{R_T + R_L + R_M} - \frac{V_T}{R_T + R_L}}{\frac{V_T}{R_T + R_L}} \times 100 = \frac{-100R_M}{R_T + R_L + R_M}$$

Loading Errors in Voltmeters

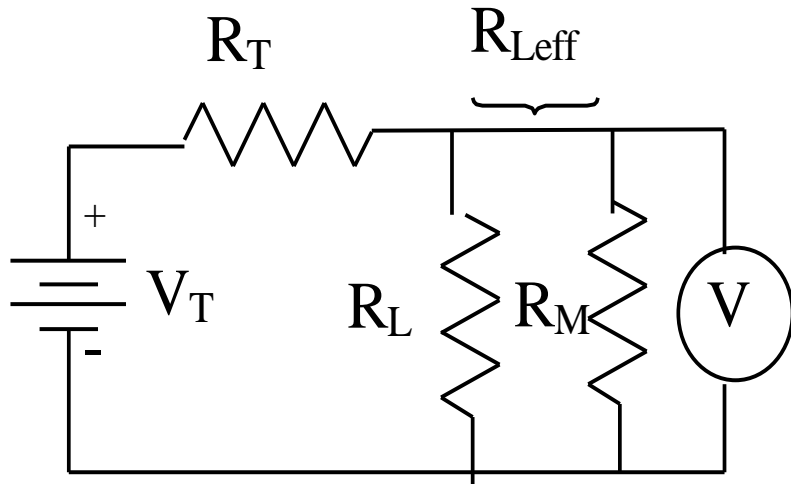

$$V_{LT} = \frac{V_T R_L}{R_T + R_L}$$


$$R_{Leff} = \frac{R_L R_M}{R_L + R_M}$$

$$V_L = V_{Lind} = \frac{V_T \frac{R_L R_M}{R_L + R_M}}{R_T + \frac{R_L R_M}{R_L + R_M}}$$

$$\% \text{ loading error} = \frac{V_{Lind} - V_{LT}}{V_{LT}} \times 100$$

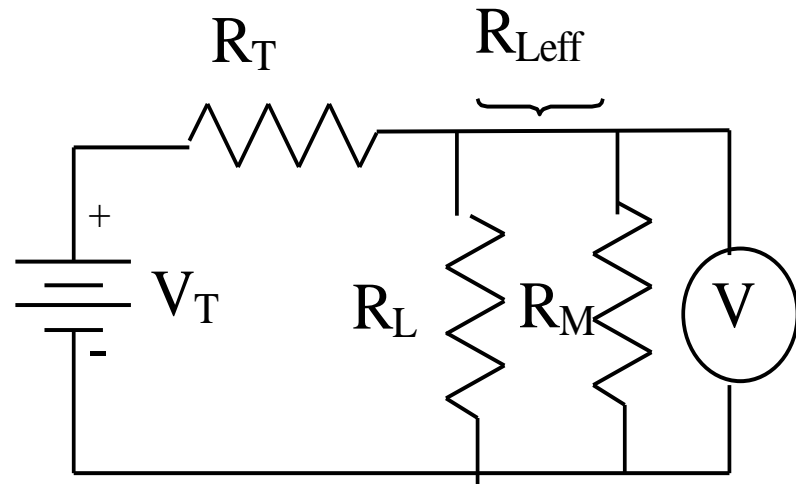Example

- A voltmeter has a resistance of $20 \text{ k}\Omega/\text{V}$ is used to measure the voltage on the circuit shown on a 0-10 V range. Find the percentage loading error. Let $R_T = R_L = 10 \text{ k}\Omega$.



Suggested Readings and Exercises

- Hughes textbook – 6.4, 6.6, 6.7, 46.2, 46.3, 46.4, 46.5
- Exercise 46 (Hughes)
 - Problems 1, 2, 5, 6, 7, 8, 9